

UESTC 3031: Engineering Project Management & Finance: Design for Manufacturing Lecture DFM 3: Process Capability

Dr Duncan Bremner



Design for Manufacturing How to use process information...


Last Lecture: Demonstrated how to characterise a process and use process capability chart

This lecture will apply this knowledge to improve your circuit designs...

1. Summarise the process capability analysis
2. Look at where you can obtain process data from literature
3. Apply data to a real design
4. Use statistical 'tricks' to improve the circuit performance.



Capability Chart Summarised

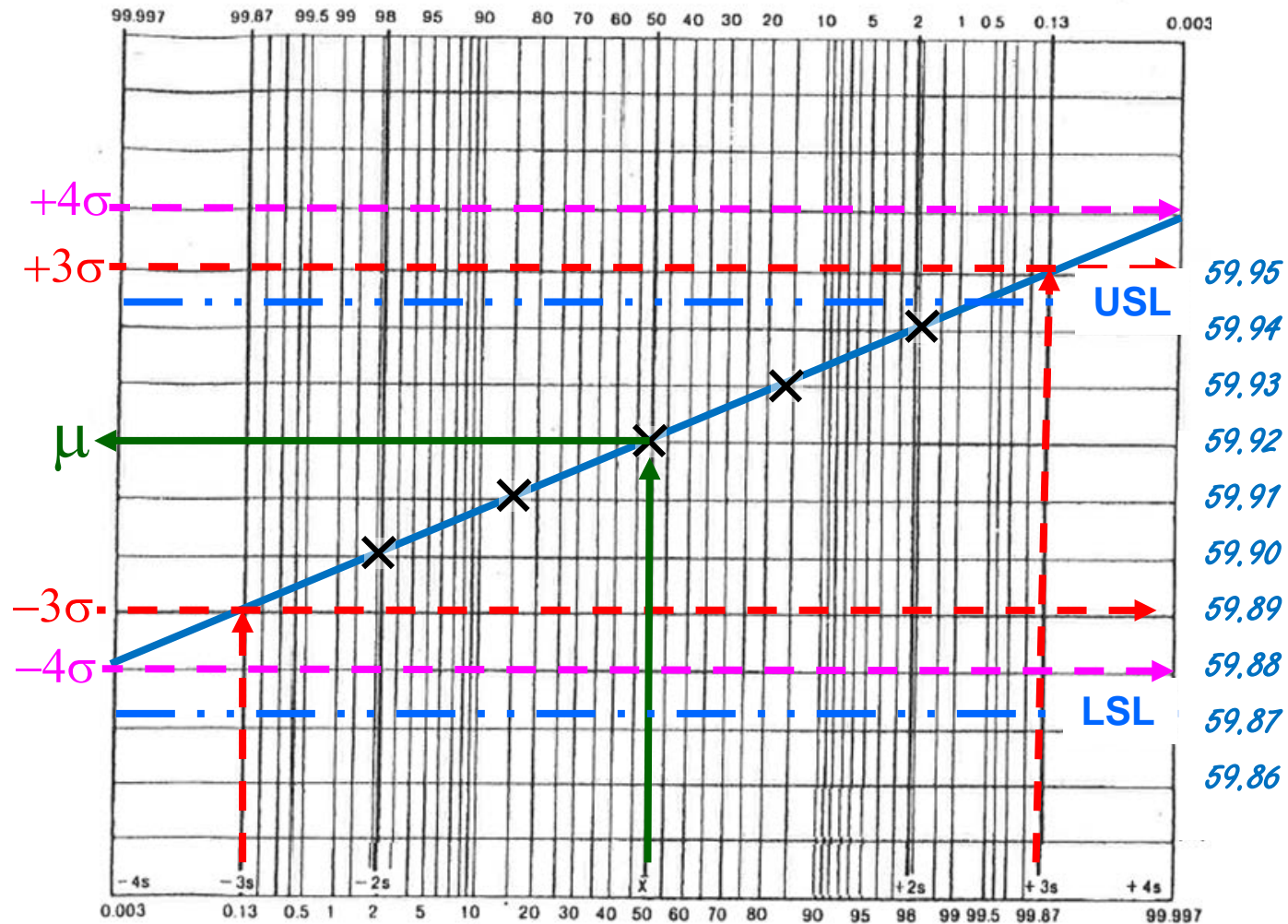

Information from Datasheets

electrical characteristics at $V_{DD} = 5\text{ V}$, $T_A = 25^\circ\text{C}$ (unless otherwise noted)

PARAMETER	TEST CONDITIONS	TLV2721Y			UNIT
		MIN	TYP	MAX	
V_{IO} Input offset voltage	$V_{DD} \pm \pm 1.5\text{ V}$, $V_{IC} = 0$, $V_O = 0$, $R_S = 50\ \Omega$		610		μV
I_{IO} Input offset current			0.5	60	μA
I_{IB} Input bias current			1	60	μA

1 σ typ figure


Example: TLV 2721 Op Amp

- You can extract information from datasheets AND perform capability analysis

Be careful...


- Worst case (Min/Max) limits STILL apply**
- But you can statistically get improved performance (See SLOA 059 in Reading list)

+/- 1 σ typ figure

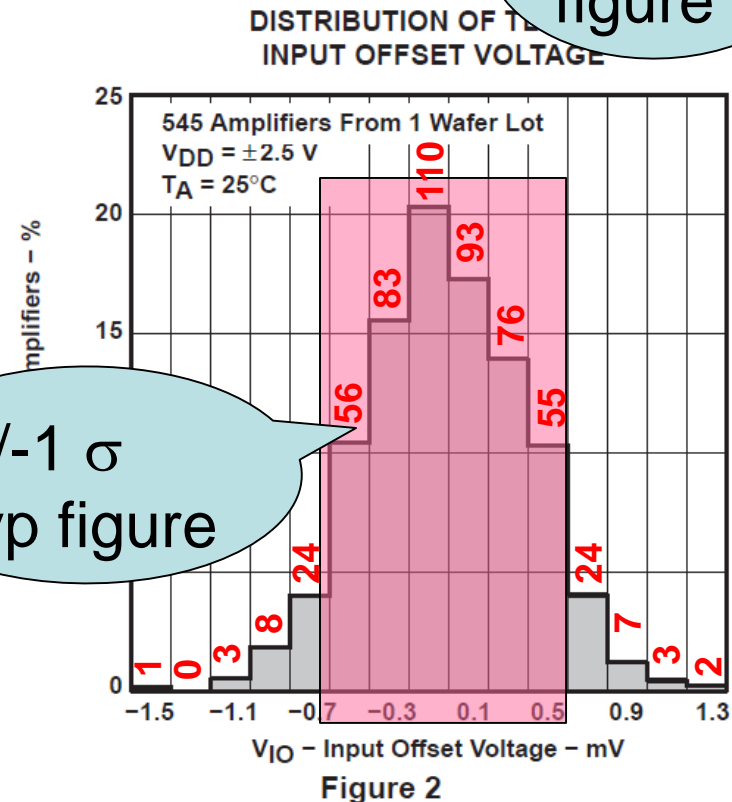



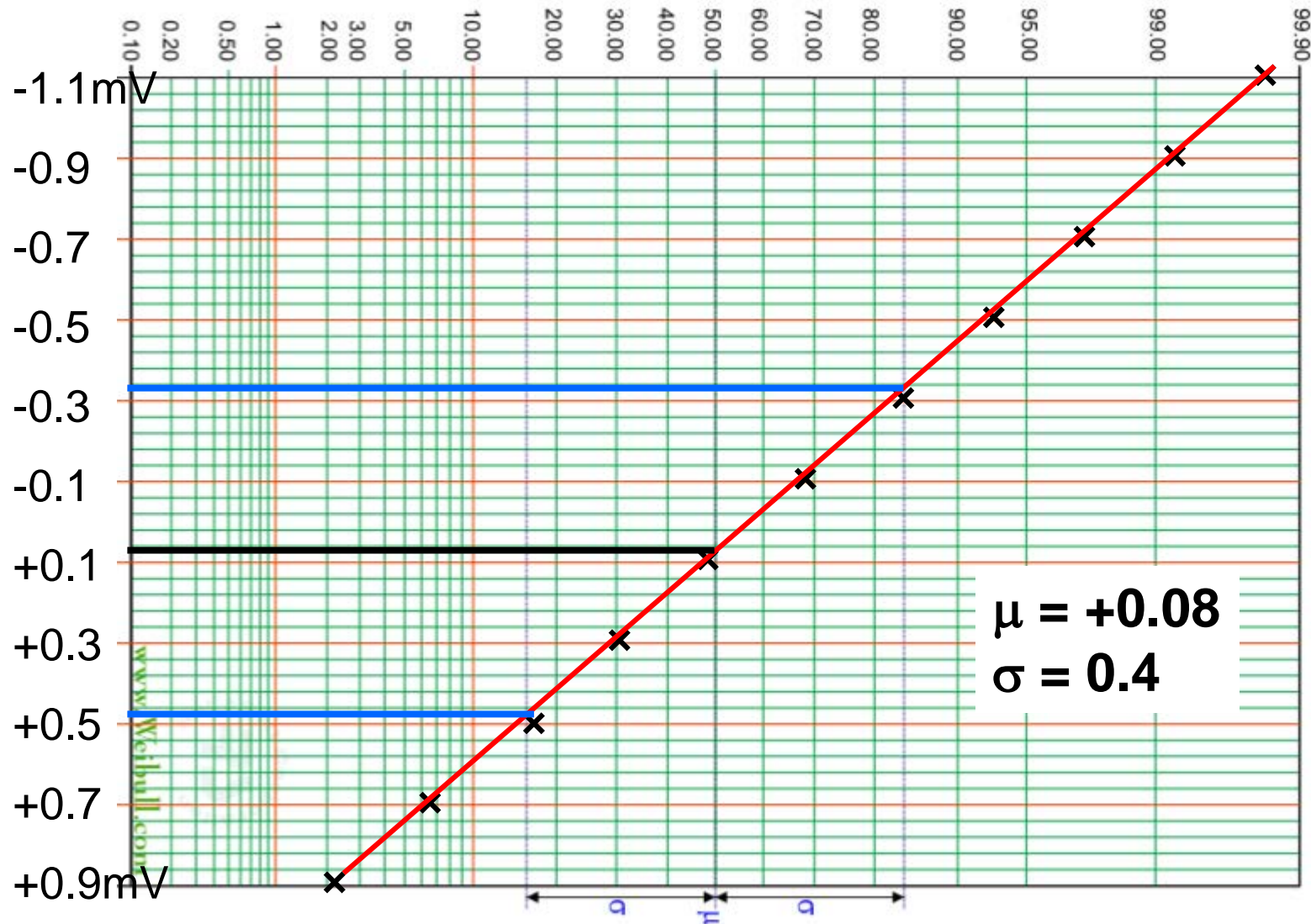Plot results to determine Mean(μ) and SD(σ)



Addition or subtraction

If $Q = a + b + c$

Use absolute numbers (ohms, V etc)

Then $\sigma_Q = \sqrt{(\sigma_a)^2 + (\sigma_b)^2 + (\sigma_c)^2}$

Multiply or Divide


If $Q = a . b . c \text{ or } a/b$

Use relative numbers (%)

$$\sigma_Q = \sqrt{\left(\left(\frac{\sigma_a}{a}\right)^2 + \left(\frac{\sigma_b}{b}\right)^2 + \left(\frac{\sigma_c}{c}\right)^2\right)}$$



Revisit our simple amplifier..

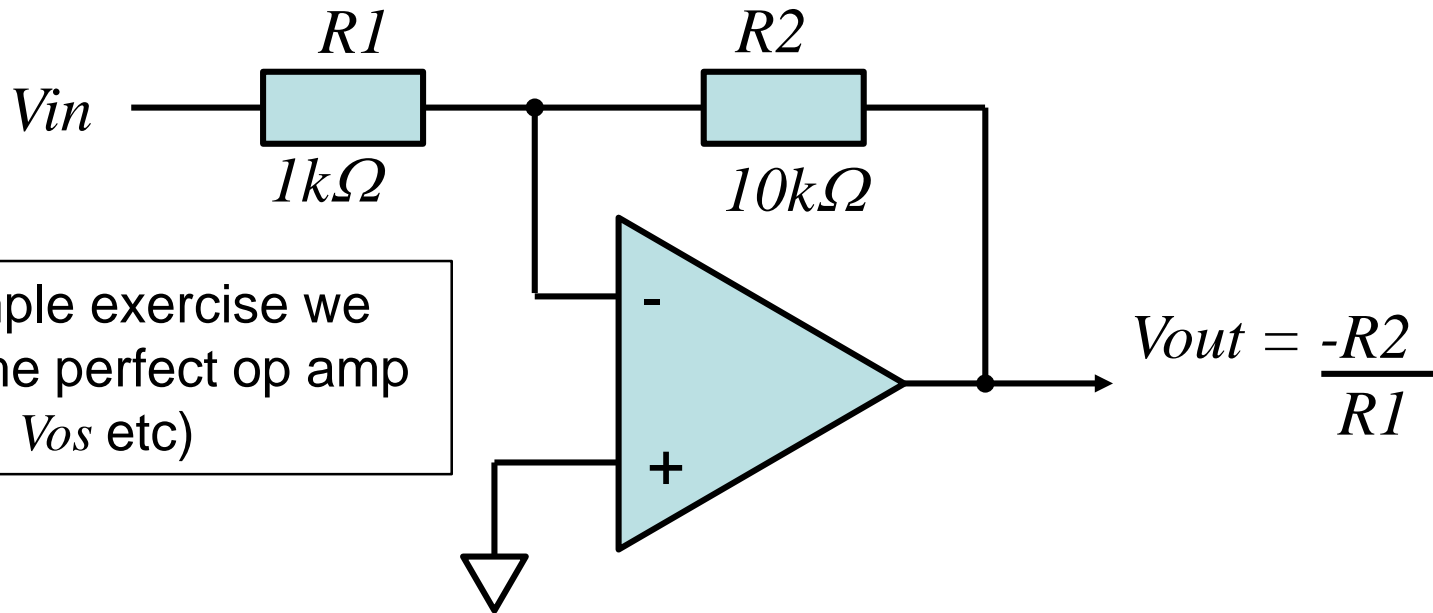

In this simple exercise we will assume perfect op amp (no I_b , I_{os} , V_{os} etc)

If we use resistors with 10% tolerance (3σ limit), how many amplifiers will have a gain of -10 ± 0.5 ? (i.e. $-10 \pm 5\%$)

Calculating the number of amplifiers

Since gain equation is:- $V_{out} = -\frac{R2}{R1}$

We use the second equation $\sigma V_{out} = \sqrt{\left(\left(\frac{\sigma_a}{R1}\right)^2 + \left(\frac{\sigma_b}{R2}\right)^2\right)}$

If Resistors are 10% tolerance


(3σ) then $1\sigma = 3.33\%$ $\sigma V_{out} = \sqrt{((0.0333)^2 + (0.0333)^2)}$

$$\sigma V_{out} = 0.047 = 4.7\%$$

If $1\sigma = 4.7\%$ then $5\% = 1.06\sigma$

Referring to probability tables $z=1.06 \Rightarrow 0.35543$

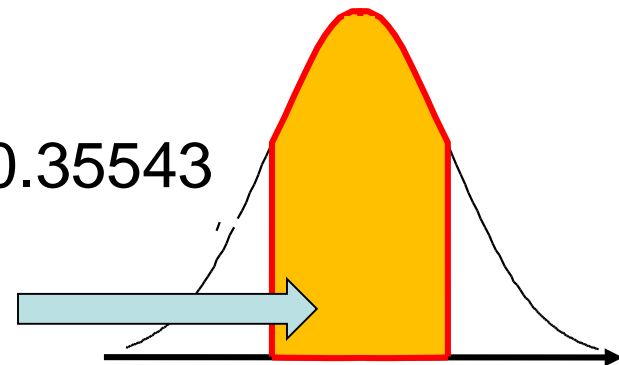
Since we want $\pm 5\%$ then $2 * 0.355 = 0.71$



Therefore 71% amplifiers have gain of -10, $\pm 5\%$



Analysing Non-inverting amplifier

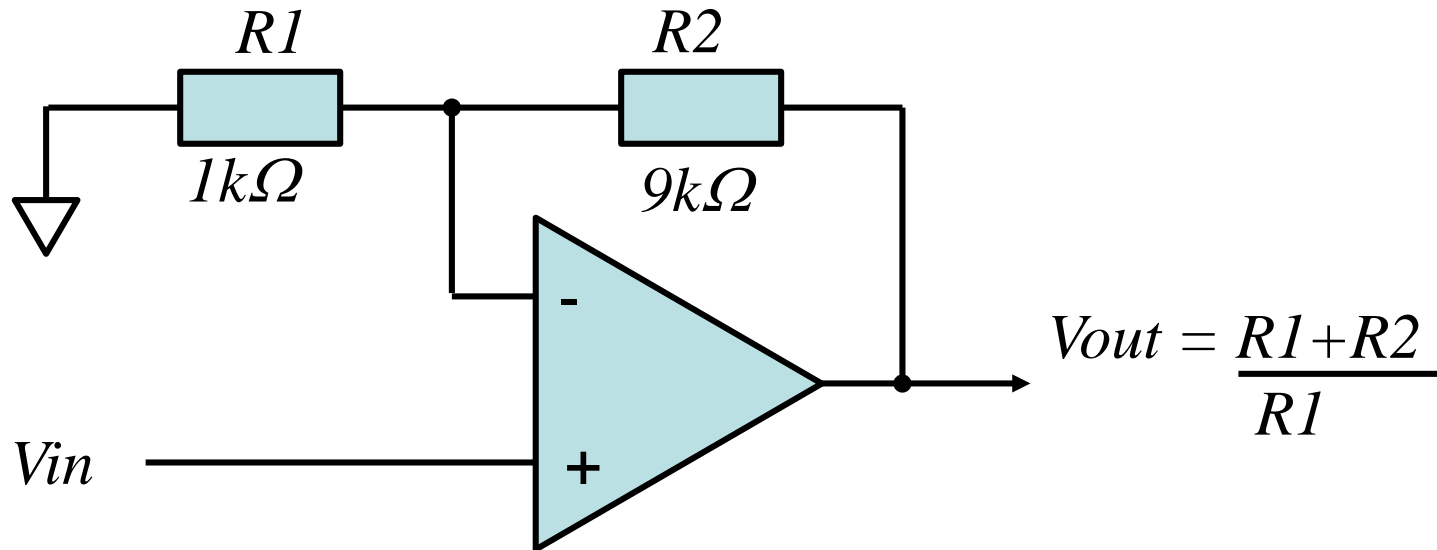

The calculation involves Addition AND division of σ

Assume all resistors are 10% tolerance

Non-Inverting (contd 2)

Calculate variation of $R1+R2 = 1K + 9K$

If 10% (3σ) resistors then $R1 \sigma = 33.3\Omega$, $R2 \sigma = 300\Omega$

Combined $\sigma = \sqrt{33.3^2 + 300^2} = 301.84 \Omega$

Convert to % error = 3.02% and then use division formula

$$\sigma Q = \sqrt{\left(\left(\frac{\sigma_a}{R1}\right)^2 + \left(\frac{\sigma_b}{R1 + R2}\right)^2\right)} = \sqrt{0.0333^2 + 0.0302^2} = 0.045$$

Therefore, 1σ Non-Inv amplifier gain error is 4.5%

Non- Inv Amplifier (contd 3)

If, 1σ Non-Inv amplifier gain error is $\pm 4.5\%$

Need to calculate proportion of amplifiers within $\pm 5\%$

$$z = 5/4.5 = 1.11$$

Referring to Probability tables, for $z = 1.11$, $P = 0.36650$

So 73.3% of amplifiers have gain of $\pm 5\%$

Circuit tricks to improve performance

Our analysis shows only ~70% of amplifiers meet spec

Can we improve this using the same grade of components?

We know... $Q = a + b + c + d$

And... $\sigma_Q = \sqrt{\sigma_a^2 + \sigma_b^2 + \sigma_c^2 + \sigma_d^2}$

If we let $R_a = R_b = R_c = R_d$ (assume 10% tolerance)

For 1000Ω resistor can use 4 x 250Ω (10%; $\sigma = 3.33\% = 8.325\Omega$)

$$\sigma_Q = \sqrt{\sigma_a^2 + \sigma_b^2 + \sigma_c^2 + \sigma_d^2} = \sqrt{4 \cdot \sigma^2} = 16.653\Omega$$

$$\sigma_Q = \sqrt{\sigma_a^2 + \sigma_b^2 + \sigma_c^2 + \sigma_d^2} = \sqrt{4 \cdot \sigma^2} = 16.653\Omega$$


The above σ is for 4 x 250 Ω resistors (=1k Ω)

By using 4 x 250 Ω resistors in series the $\sigma = 16.653\Omega$ (1.65%)

Using a single 1k Ω resistor, $\sigma = 33.305\Omega$ (3.33%)

We have **improved** the resistor variation by \sqrt{N} , where N is number of resistors (can be in series or parallel)

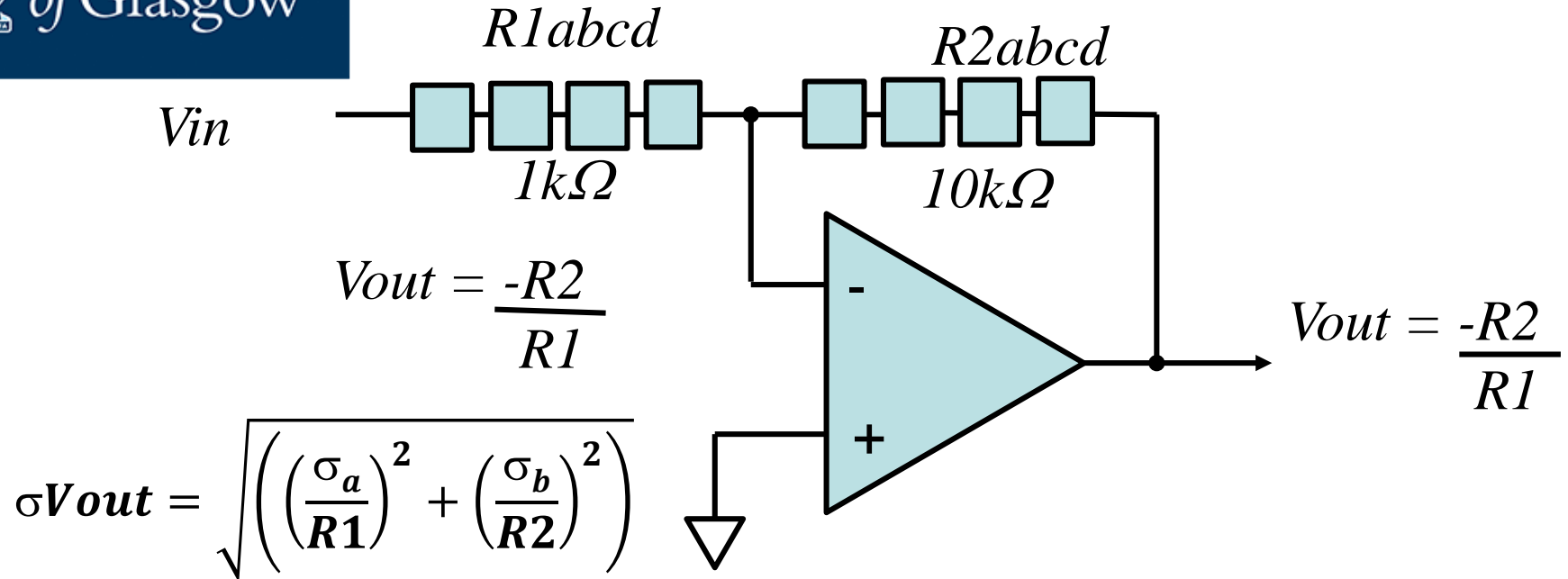Now apply this approach to the amplifier...



If Resistors are 10% tolerance, we get a \sqrt{N} improvement

$$\sigma V_{out} = \sqrt{((0.0165)^2 + (0.0165)^2)}$$

$$\sigma V_{out} = 0.0235 = 2.3\%$$

How many amplifiers now?

If new $\sigma V_{out} = 0.0235 = 2.35\%$

Need to calculate proportion of amplifiers within +/- 5%

$$z = 5\% / 2.35\% = 2.13$$

Referring to Probability tables, for $z = 2.13$, $P = 0.48341$

So now, 96.7% of amplifiers have gain of -10, +/-5%

**We are only losing 3.3% of amplifiers now...
= \$\$\$\$\$\$!!!!**

- We have looked at the Process capability
- We have seen how data can be extracted from datasheets for analysis
- Component variation has been incorporated into circuit design
- You have been shown circuit ‘tricks’ to improve the performance using low cost components
- Next lecture
 - We look at Six sigma design

TLV2721 Datasheet

Probability Tables



University
of Glasgow

Thank you
谢谢

